

# 20 Watt Simple Switcher Forward Converter

National Semiconductor  
 Application Note 776  
 Frank DeStasi  
 Tom Gross  
 April 1998



A 20W, 5V at 4A, step-down regulator can be developed using the LM2577 Simple Switcher IC in a forward converter topology. This design allows the LM2577 IC to be used in step-down voltage applications at output power levels greater than the 1 A LM2575 and 3 A LM2576 buck regulators. In addition, the forward converter can easily provide galvanic isolation between input and output.

The design specifications are:

$V_i$ Range	:20V–24V
$V_o$	:5V
$I_{o(max)}$	4A
$\Delta V_o$	:20 mV

With the input and output conditions identified, the design procedure begins with the transformer design, followed by the output filter and snubber circuit design.

### TRANSFORMER DESIGN

1. Using the maximum switch voltage, input voltage, and snubber voltage, the transformer's primary-to-clamp windings turns ratio is calculated:

$$V_{SW} \geq V_{imax} + V_{imax} (N_p/N_c) + V_{snubber}$$

$$N_p/N_c \leq (V_{SW} - V_{imax} - V_{snubber})/V_{imax}$$

$$N_p/N_c \leq (60V - 24V - 5V)/24V = 1.29$$

Let  $N_p/N_c = 1.25$

The  $V_{snubber}$  voltage is an estimate of the voltage spike caused by the transformer's primary leakage inductance.

2. The duty cycle,  $t_{on}/T$ , of the switch is determined by the volt-second balance of the primary winding.

During  $t_{on}$ :

$$V_i = L_p (\Delta i / T_{ON}) \rightarrow \Delta i = (V_i / L_p) t_{on}$$

During  $t_{off}$ :

$$V_i = (N_p/N_c) L_p (\Delta i / t_{off}) \rightarrow \Delta i = (N_p/N_c) (V_i / L_p) t_{off}$$

Setting  $\Delta i$ 's equal;

$$(V_i / L_p) t_{on} = (N_p/N_c) (V_i / L_p) t_{off}$$

$$t_{on}/t_{off} = N_p/N_c$$

$$\text{Since } D = t_{on}/T = t_{on}/(t_{on} + t_{OFF})$$

$$\text{max. duty cycle} = D_{max} = (N_p/N_c) / [(N_p/N_c) + 1]$$

$$D_{max} = (1.25) / (1.25 + 1) = 0.56 \text{ (56\%)}$$

3. The output voltage equations of a forward converter provides the transformer's secondary-to-primary turns ratio:

$$V_o + V_{diode} \leq V_{imin} \times D_{max} (N_s/N_p)$$

$$N_s/N_p \geq (V_o + V_{diode}) / (V_{imin} \times D_{max})$$


$$N_s/N_p \geq (5.5V) / (20V)(56\%) = 0.49$$

$$\Delta \text{let } N_s/N_p = 0.5$$

4. Calculate transformer's primary inductance by finding the maximum magnetizing current ( $\Delta i_{Lp}$ ) that does not allow the maximum switch current to exceed it's 3 A limit (capital I for DC current,  $\Delta i$  for AC current, and lower case i for total current):

$$i_{sw} = i_{pri} = i_{Lo} + \Delta i_{Lp}$$

Basic Forward Converter

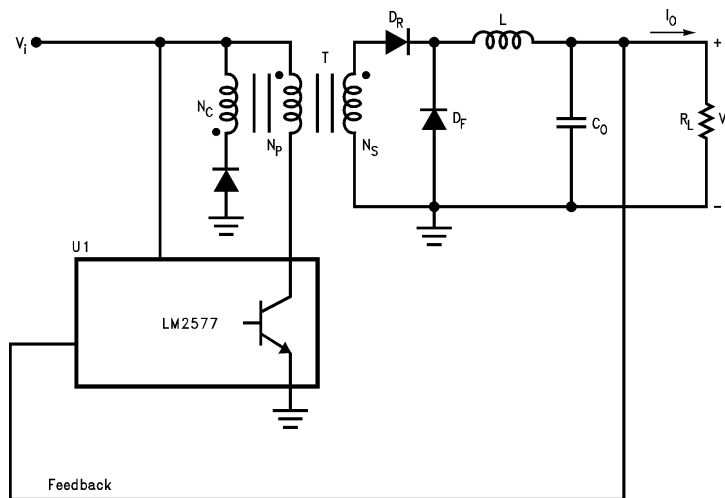

AN011216-1

where  $i_{L_o}$  is the reflected secondary current and  $\Delta i_{L_p}$  is the primary inductance current.

$$i_{L_o'} = i_{L_o}(N_s/N_p) \quad (i_{L_o} \text{ reflected to primary})$$

$$i_{L_o} = I_{L_o} \pm \Delta i_{L_o}/2$$

$\Delta i_{L_o}$  is the output inductor's ripple current

$$I_{L_o} = I_o \text{ (the load current)}$$



$$i_{L_o'} = (I_o \pm \Delta i_{L_o}/2)(N_s/N_p)$$

$$i_{L_o'(pk)} = (I_{o(max)} + \Delta i_{L_o}/2)(N_s/N_p)$$

$$i_{sw} = I_{sw} + \Delta i_{sw}$$

$$i_{sw(pk)} = i_{L_o'(pk)} + \Delta i_{L_p(pk)}$$

$$i_{sw(pk)} = (I_{o(max)} + \Delta i_{L_o}/2)(N_s/N_p) + \Delta i_{L_p(pk)}$$

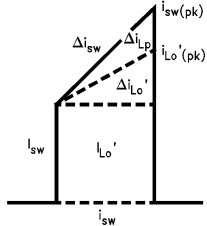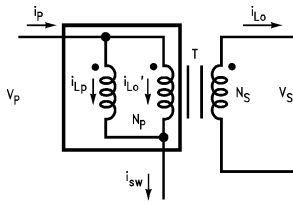

AN011216-2

Using standard inductors, a good practical value to set the output inductor current ( $\Delta i_{L_o}$ ) to is 30% of the maximum load current ( $I_o$ ). Thus;

$$i_{sw(pk)} = (I_{o(max)} + 0.15\Delta i_{L_o})(N_s/N_p) + \Delta i_{L_p(pk)}$$

$$\Delta i_{L_p(pk)} = i_{sw(pk)} - (I_{o(max)} + 0.15\Delta i_{L_o})(N_s/N_p)$$

$$\Delta i_{L_p(pk)} = 3A - (4A + 0.15 \times 4A)(0.5) = 0.7A$$

$$L_p = V_{pri} \times \Delta t / \Delta i = (V_i - V_{sat})(t_{on} / \Delta i_{L_p(pk)})$$

$$= (V_{i(max)} - V_{sat})(D_{max} / (\Delta i_{L_p(pk)} \times f))$$

$$= (24V - 0.8V)(0.56 / 0.7 \times 52 \text{ kHz})$$

$$L_p = 357 \mu H$$

$$\Delta \text{let } L_p = 350 \mu H$$

### OUTPUT FILTER — INDUCTOR

The first component calculated in the design is the output inductor, using the current-to-voltage relationship of an inductor:

$$V_L = L_o (\Delta i_{L_o} / t_{on})$$

Choosing an inductor ripple current value of  $0.3I_o$  and a maximum output current of 4A:

$$\Delta i_{L_o} = 0.3 (4A) = 1.2A$$

During  $t_{on}$ :

$$V_L = V_s - V_D - V_o \text{ [where } V_s = (V_i - V_{sat})(N_s/N_p)\text{]}$$

Thus,


$$[(V_i - V_{sat})(N_s/N_p) - V_d - V_o] = L_o (\Delta i_{L_o} / D) f$$

$$L_o = [(V_i - V_{sat})(N_s/N_p) - V_d - V_o] \times D / \Delta i_{L_o} \times f$$

$$L_o = [(24V - 0.8V)(0.5) - 0.5V - 5V] 56\% / 1.2A \times 52 \text{ kHz}$$

$$L_o = 55 \mu H$$

$$\Delta \text{let } L_o = 60 \mu H$$

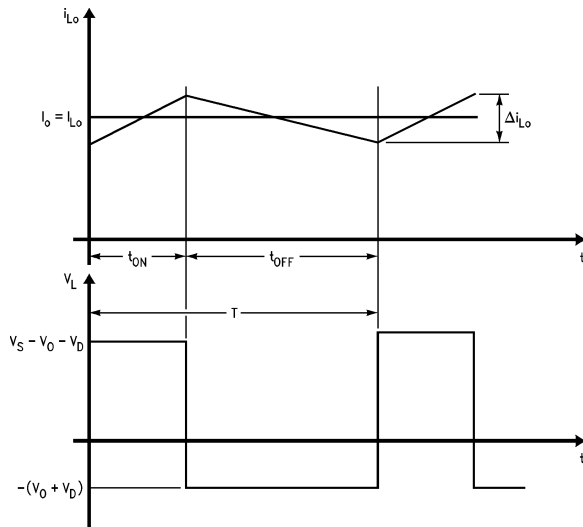

AN011216-3

### OUTPUT FILTER — CAPACITOR

Since the output capacitor's current is equal to inductor's ripple current, the output capacitor's value can be found using the inductor's ripple current. Starting with the current-voltage relationship, the output capacitance is calculated:

$$\begin{aligned}\Delta V_o &= 1/C_o \int i dt \\ &= \Delta i_{L_o} / 4C_o (TR/2) \\ &= (\Delta i_{L_o} \cdot T) / 8C_o \\ C_o &= (\Delta i_{L_o} \cdot T) / 8\Delta V_o\end{aligned}$$

However, the equivalent series resistance (ESR) of the capacitor multiplied by the inductor's ripple current creates a parasitic output ripple voltage equal to:

$$\Delta V_o = ESR_{CO} \cdot \Delta i_{L_o} = ESR_{CO} \cdot 0.3 I_o$$

This parasitic voltage is usually much larger than the inherent ripple voltage. Hence, the output capacitor parameter of interest, when calculating the output ripple voltage, is the equivalent series resistance (the capacitance of the output capacitor will be determined by the frequency response analysis). Using a standard-grade capacitor with ESR of 0.05Ω produces a total output ripple voltage of:

$$\Delta V_o = 0.05\Omega \cdot 1.2A \approx 60 \text{ mV}$$

To get output ripple voltage of 20 mV or less (as was part of the design specs) requires a capacitor with ESR of less than 17 mΩ.

### SNUBBER CIRCUIT

A snubber circuit ( $C_S$ ,  $R_S$ ,  $D_S$ ) is added to reduce the voltage spike at the switch, which is caused by the transformer's leakage inductance. It is designed as follows: when the switch is off,

$$\begin{aligned}V_R &= V_{CE} - V_{IN} - V_D \\ V_{LL} &= V_D + V_R - V_{IN}(N_p/N_c)\end{aligned}$$

Substituting for  $V_R$ , the voltage across the leakage inductance,  $V_{LL}$ , is,

$$V_{LL} = V_{CE} - V_{IN}(1 + N_p/N_c)$$

Using the current-voltage relationship of inductors,

$$t_S = I_{PRI}(L_L/V_{LL})$$

Substituting for  $V_{LL}$ ,

$$t_S = I_{PRI} L_L / (V_{CE} - V_{IN}(1 + N_p/N_c))$$

Calculating for the average leakage inductance current,  $I_{LL(AVE)}$ ,

$$\begin{aligned}I_{LL(AVE)} &= I_{PRI(MAX)} (t_S)/2T \\ &= I_{PRI(MAX)}^2 L_L f / 2(V_{CE} - V_{IN}(1 + N_p/N_c))\end{aligned}$$

Solving for the snubber resistor;

$$R_S = V_R / I_{LL(AVE)}$$

Substituting  $I_{LL(AVE)}$  and  $V_R$  results in,

$$\begin{aligned}R_S &= 2 (V_{CE} - V_{IN}(1 + N_p/N_c)) X \\ & (V_{CE} - V_{IN} - V_D) / (L_L (I_{PRI(MAX)})^2 f)\end{aligned}$$

Choosing  $L_L$  to equal 10% of  $L_p$ ,

$$\begin{aligned}R_S &= 2 (65V - 24V - 1V) X (65V - 24V(2.25)) / \\ & (7 \mu H (3A)^2 52 \text{ kHz}) \\ & = 268.9\Omega \approx 270\Omega\end{aligned}$$

Using the current-voltage relationship of capacitors,

$$\Delta V_R = (T - t_S) I_C / C_S = (T - t_S) V_R / R_S C_S \approx V_R / R_S C_S f$$

The capacitor  $C_S$  equates to,

$$C_S = V_R / R_S f \Delta V_R$$

$$C_S = 40V / (270\Omega)(52 \text{ kHz}) 10V = 0.28 \mu F \approx 0.33 \mu F$$

The snubber diode has a current rating of 1A peak and a reverse voltage rating of 30V.


### OTHER COMPONENTS

Diodes,  $D_R$  and  $D_F$ , used in the secondary are 5A, 30V Schottky diodes. The same diode type is used for  $D_C$ , however a lower current diode could have been used.


A compensation network of  $R_C$  and  $C_C$  optimizes the regulator's stability and transient response and provides a soft-start function for a well-controlled power-up.

The finished circuit is shown below.

5V, 4 A Forward Converter Circuit Schematic

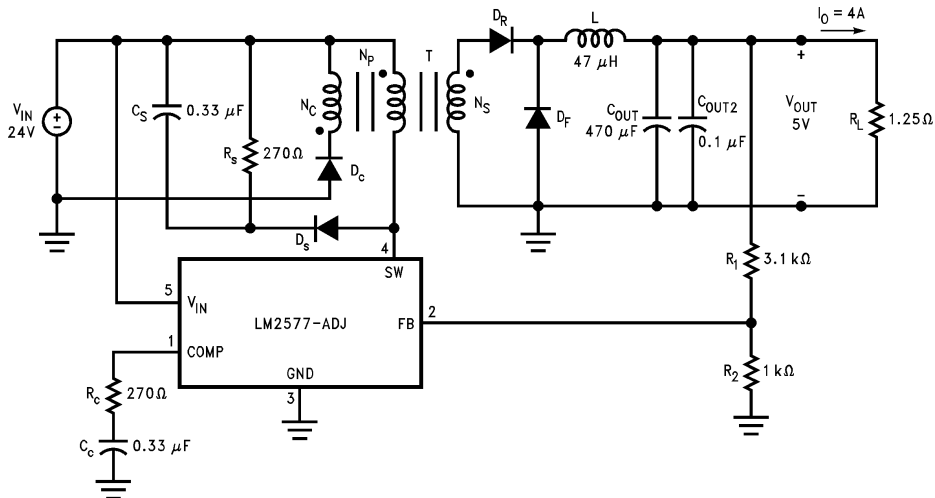


AN011216-4

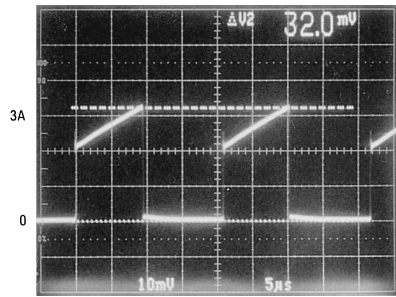


Vertical: 1 A/div  
Horizontal: 5 μs/div

**Switch Current**

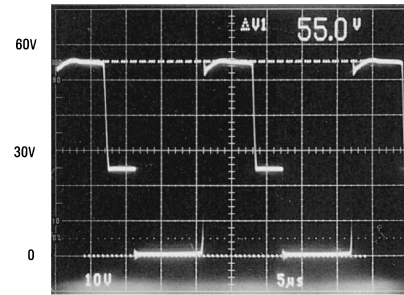


Vertical: 10 V/div  
Horizontal: 5 μs/div

**Switch Voltage**

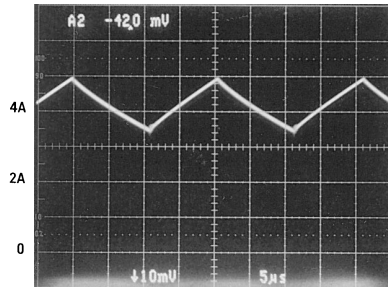


Vertical: 1 A/div  
Horizontal: 5 μs/div

**Inductor Current**

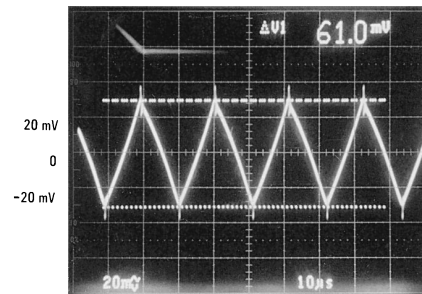

Vertical: 20 mV/div  
Horizontal: 10 μs/div

**Output Ripple Voltage**

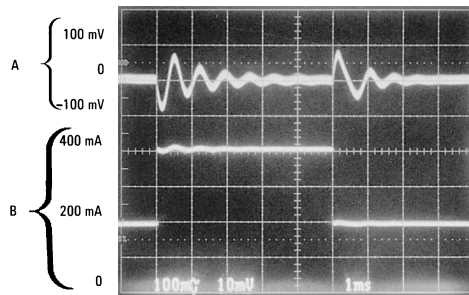

A: Output Voltage Change, 100 mV/div  
B: Output Current, 200 mA/div  
Horizontal: 10 ms/div

**Load Step Response**





**LIFE SUPPORT POLICY**

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component in any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
Americas  
Tel: 1-800-272-9959  
Fax: 1-800-737-7018  
Email: support@nsc.com

[www.national.com](http://www.national.com)

**National Semiconductor Europe**  
Fax: +49 (0) 1 80-530 85 86  
Email: europe.support@nsc.com  
Deutsch Tel: +49 (0) 1 80-530 85 85  
English Tel: +49 (0) 1 80-532 78 32  
Français Tel: +49 (0) 1 80-532 93 58  
Italiano Tel: +49 (0) 1 80-534 16 80

**National Semiconductor Asia Pacific Customer Response Group**  
Tel: 65-2544466  
Fax: 65-2504466  
Email: sea.support@nsc.com

**National Semiconductor Japan Ltd.**  
Tel: 81-3-5620-6175  
Fax: 81-3-5620-6179